



Load characteristics D.C. Generator

10/3/2016

ملاحظات 3 حالات كهربية

19

Magnetization ch/s of D.C. Generators

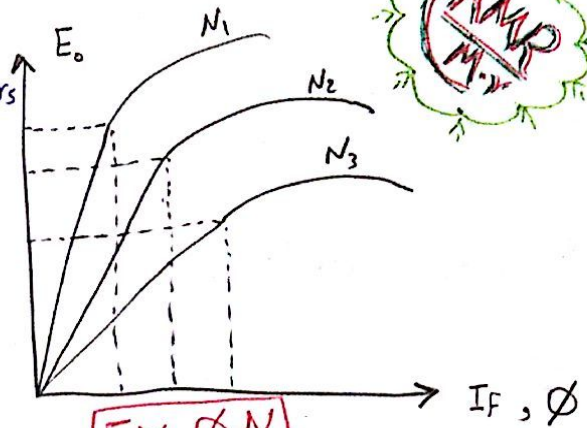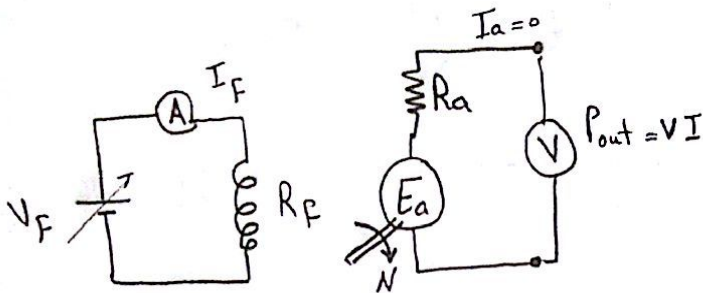

| | | | | | | | | | | |
|-------|---|----|----|----|-----|-----|-----|-----|-----|-----|
| I_F | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 |
| E_a | 1 | 50 | 70 | 90 | 100 | 120 | 130 | 135 | 137 | 140 |

$$E = \frac{P}{A} \cdot \Phi \cdot Z \cdot \frac{N}{60}$$

* Load characteristics D.C. Generator.

[a]- Internal ch/s (I_a, E_a).

[b]- external ch/s (I_L, V_t).

1) shunt D.C. Generator


$$I_a = I_L + I_{sh}$$

$$I_{sh} = \text{const} = \frac{V}{R_{sh}}$$

$$E = \frac{P}{A} \cdot Z \cdot \frac{N}{60} \cdot \Phi$$


$$(\Phi_{sh} - \Phi_{A.R})$$

$$\Phi_{AR} \ll \Phi_F$$

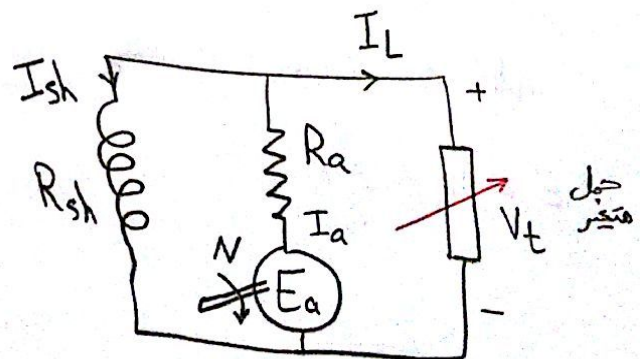

جهد متغير


b

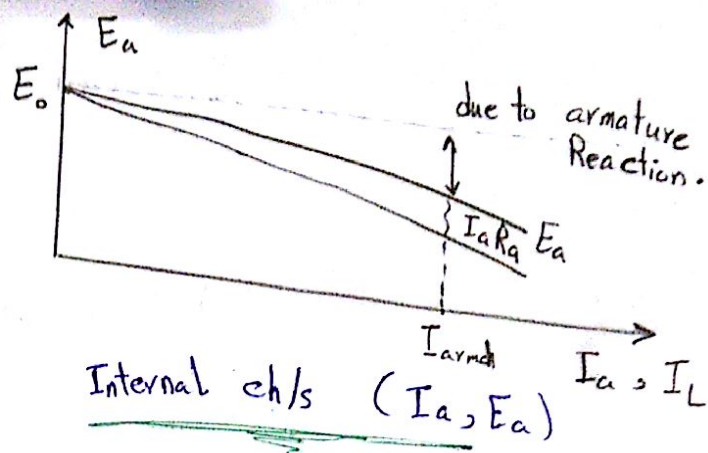

* External ch/s of D.C. shunt Generators (I_L, V_t).

$$V_t = E_a - I_a R_a - \Delta V_b$$


ΔV_b
لا يقاوم
جدا



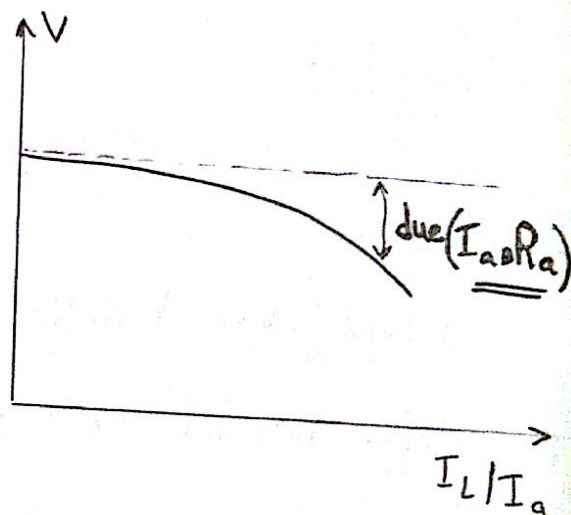


[2] Series Generators.

at No load $\underline{I_a = 0} \rightarrow \infty E \approx 0$
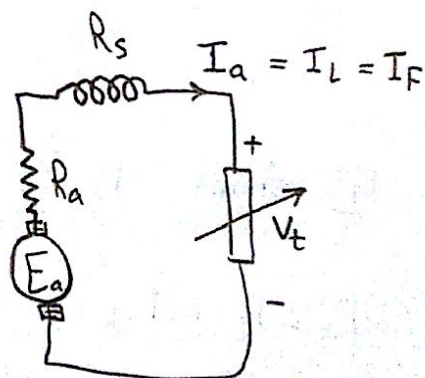
$$E = \frac{P}{A} \times \frac{Z N}{60}$$



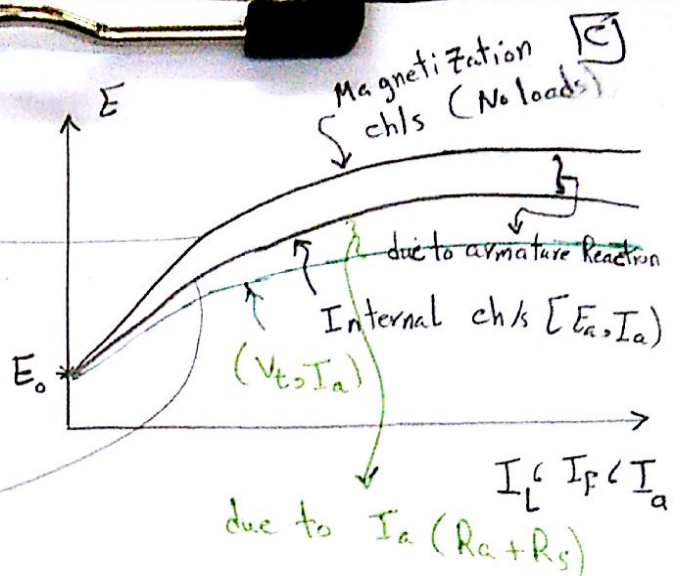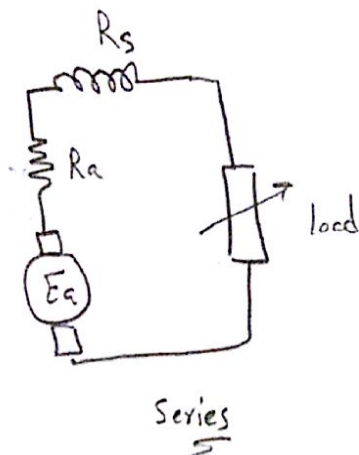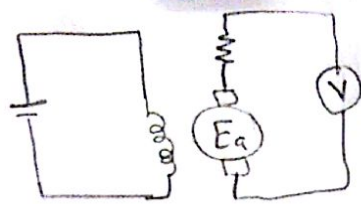

$$V_t = E_a - I_a(R_a + R_s)$$


[3] Compound Generator

$$I_a = I_L + I_{sh}$$

$$\phi_f = \phi_{sh} \pm \phi_R$$

$$\phi_T = (\phi_{sh} + \underbrace{\phi_s - \phi_{AR}}_{I_a \text{ of } R_s})$$

[a] over compound $\phi_s > \phi_{A.R}$

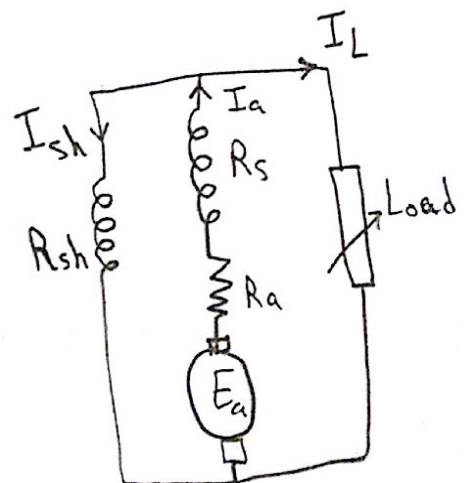


d)

Comalative



Case [a]

[a]

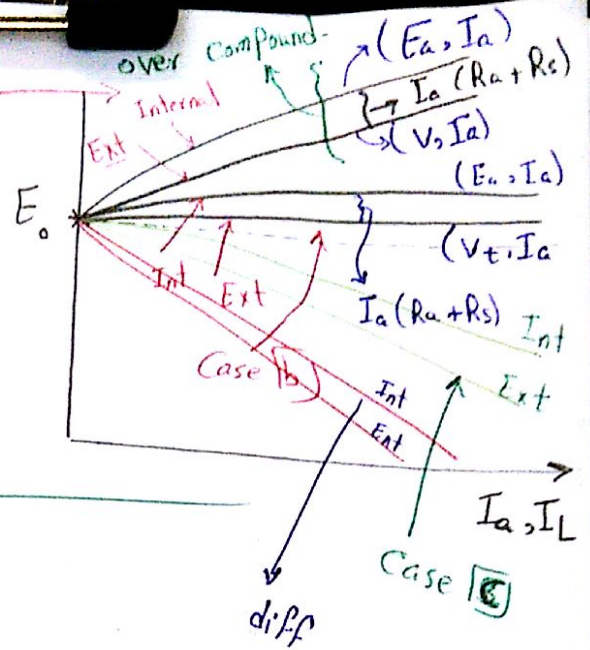

[b] Flat compound



$$\phi_t = \phi_{sh} + \underbrace{\phi_s - \phi_{AR}}_{\rightarrow I_a \text{ decreases}}$$

[c] under compound

$$\phi_t = \phi_{sh} + \phi_s - \phi_{AR} \quad \text{where } \phi_s < \phi_{AR}$$

$$\text{diff} \rightarrow \phi_t = \phi_{sh} - \underbrace{\phi_s}_{I_a} - \phi_{AR}$$

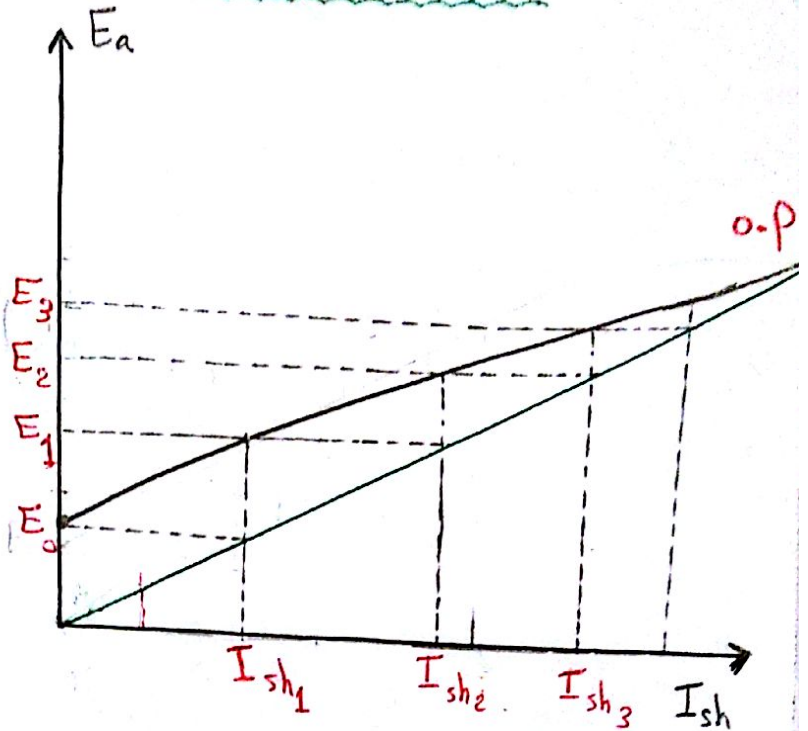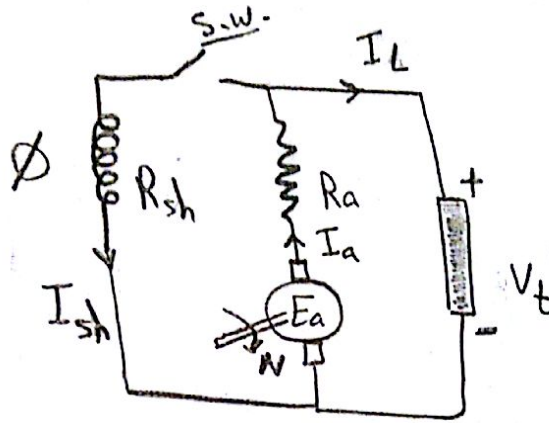Voltage Building in self Excited Generators.



$$E_o = \frac{P}{A} \Phi R Z \frac{N}{60}$$

* في حالة الدورات مع فتح المفتاح -

← إذا كانت الدالة أول مرة تعمل يكون الفيض المتولد $E_a = \text{Zero}$
 ← إذا كان هناك تفاعل فيهما مختزن في الحديد يكون الفيض المتولد $E_a = E_o$

* في حالة غلق المفتاح -

← يكون الفيض هو المحصل الفيض المختزن في الحديد بالإضافة إلى الفيض المتولد من R_{sh}
 و بذلك يزداد قيمة E_a وبالتالي يزداد قيمة التيار I_a

* في حالة إزالة الحمل R_{load} ← يكون فرق الجهد المتولد

$$E_a = I_f R_{sh}$$